


Last updated on July 18th, 2017 at 09:26 pm

Contents


- 1 BCD to 7 Segment Decoder
- 2 BCD to 7 segment display Decoder Truth Table
- 3 BCD to 7 segment display Decoder Circuit
- 4 VHDL Code for BCD to 7 segment display using Combinatorial logic
- 5 VHDL Code for BCD to 7 segment display using Case Statement
- 6 VHDL Testbench Code for BCD to 7 segment display
- 7 Testbench waveform for BCD to 7 Segment Display Decoder

BCD to 7 Segment Decoder

 The BCD to 7 Segment Decoder converts 4 bit binary to 7 bit control signal which can be displayed on 7 segment display. Seven display consist of 7 led segments to display 0 to 9 and A to F.



 VHDL Code BCD to 7 Segment Display decoder can be implemented in 2 ways. By simplifying





Boolean expression to implement structural design and behavioral design.

For constructing BCD to 7 segment display, first construct truth table and simplify them to Boolean expression using K Map and finally build the combinational circuit.

BCD to 7 segment display Decoder Truth Table

B3 B2 B1 B0	A B C D E F G
0000	0000001
0001	1001111
0010	0010010
0011	0000110
0100	1001100
0101	0100100
0110	0100000
0111	0001111
1000	0000000
1001	0000100

BCD to 7 segment display Decoder Circuit

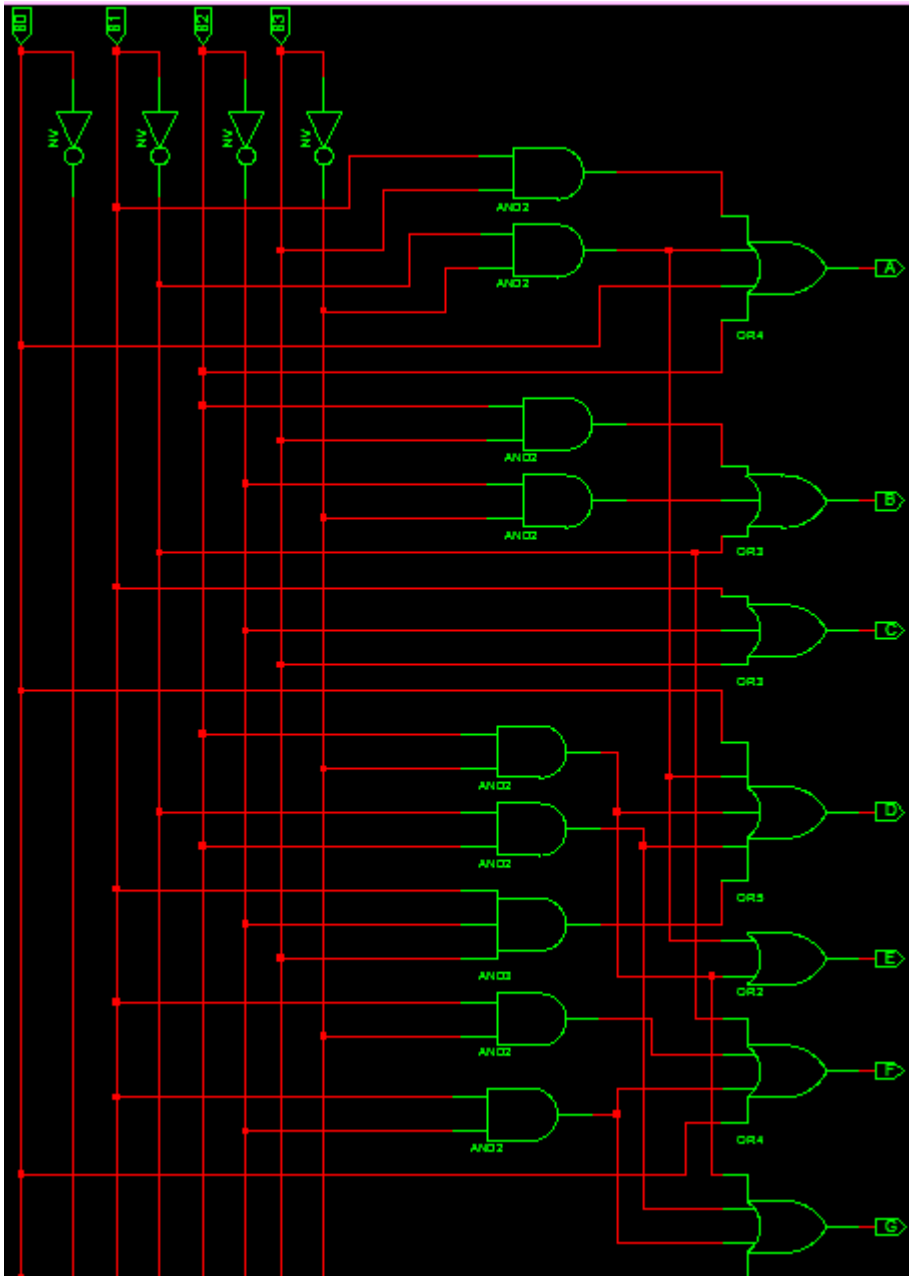 


The boolean expression for the logic circuit is

$$A = B_0 + B_2 + B_1B_3 + B_1'B_3'$$

$$B = B_1' + B_2'B_3' + B_2B_3$$

$$C = B_1 + B_2' + B_3$$

 

$$D = B1'B3' + B2B3' + B1B2'B3 + B1'B2 + B0$$

$$E = B1'B3' + B2B3'$$

$$F = B0 + B2'B3' + B1B2' + B1B3'$$

$$G = B0 + B1B2' + B1'B2 + B2B3'$$

VHDL Code for BCD to 7 segment display using Combinatorial logic


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity bcd_7seg is
Port ( B0,B1,B2,B3 : in STD_LOGIC;
A,B,C,D,E,F,G : out STD_LOGIC);
end bcd_7seg;

architecture Behavioral of bcd_7seg is

begin

A <= B0 OR B2 OR (B1 AND B3) OR (NOT B1 AND NOT B3);
B <= (NOT B1) OR (NOT B2 AND NOT B3) OR (B2 AND B3);
C <= B1 OR NOT B2 OR B3;
D <= (NOT B1 AND NOT B3) OR (B2 AND NOT B3) OR (B1 AND NOT B2 AND B3)
OR (NOT B1 AND B2) OR B0;
E <= (NOT B1 AND NOT B3) OR (B2 AND NOT B3);
F <= B0 OR (NOT B2 AND NOT B3) OR (B1 AND NOT B2) OR (B1 AND NOT B3);
G <= B0 OR (B1 AND NOT B2) OR ( NOT B1 AND B2) OR (B2 AND NOT B3);
```

 

```
end Behavioral;
```

VHDL Code for BCD to 7 segment display using Case Statement

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;


entity bcd_7segment is
Port ( BCDin : in STD_LOGIC_VECTOR (3 downto 0);
Seven_Segment : out STD_LOGIC_VECTOR (6 downto 0));
end bcd_7segment;

architecture Behavioral of bcd_7segment is

begin

process(BCDin)
begin

 case BCDin is
when "0000" =>
Seven_Segment <= "0000001"; ---0
when "0001" =>
Seven_Segment <= "1001111"; ---1
when "0010" =>
Seven_Segment <= "0010010"; ---2
when "0011" =>
Seven_Segment <= "0000110"; ---3
when "0100" =>
```



```
Seven_Segment <= "1001100"; ---4
when "0101" =>
Seven_Segment <= "0100100"; ---5
when "0110" =>
Seven_Segment <= "0100000"; ---6
when "0111" =>
Seven_Segment <= "0001111"; ---7
when "1000" =>
Seven_Segment <= "0000000"; ---8
when "1001" =>
Seven_Segment <= "0000100"; ---9
when others =>
Seven_Segment <= "1111111"; ---null
end case;

end process;

end Behavioral;
```


VHDL Testbench Code for BCD to 7 segment display

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_bcd_7seg IS
END tb_bcd_7seg;

ARCHITECTURE behavior OF tb_bcd_7seg IS

 -- Component Declaration for the Unit Under Test (UUT)
```



```
COMPONENT bcd_7segment
PORT(
BCDin : IN std_logic_vector(3 downto 0);
Seven_Segment : OUT std_logic_vector(6 downto 0)
);
END COMPONENT;

--Inputs
signal BCDin : std_logic_vector(3 downto 0) := (others => '0');


--Outputs
signal Seven_Segment : std_logic_vector(6 downto 0);

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: bcd_7segment PORT MAP (
  BCDin => BCDin,
  Seven_Segment => Seven_Segment
 );

-- Stimulus process
 stim_proc: process
 begin

   BCDin <= "0000";
  wait for 100 ns;
  BCDin <= "0001";
  wait for 100 ns;
  BCDin <= "0010";
  wait for 100 ns;
  BCDin <= "0011";
  wait for 100 ns;
  BCDin <= "0100";
```



```
wait for 100 ns;  
BCDin <= "0101";  
wait for 100 ns;  
BCDin <= "0110";  
wait for 100 ns;  
BCDin <= "0111";  
wait for 100 ns;  
BCDin <= "1000";  
wait for 100 ns;  
BCDin <= "1001";  
wait for 100 ns;  
end process;  
  
END;
```

Testbench waveform for BCD to 7 Segment Display Decoder

