


Contents

- [1 Accumulator](#)
- [2 Accumulator Block Diagram](#)
- [3 VHDL Code for 4-bit Asynchronous Accumulator](#)
- [4 TestBench VHDL Code for 4-bit Asynchronous Accumulator](#)
- [5 Output Waveform for Accumulator VHDL Code](#)

Accumulator

Accumulator work similar to the functionality of counter. The main difference is instead increment the counter value by constant, Accumulator add the input value with the current value.


Accumulator Block Diagram

 

VHDL Code for 4-bit Asynchronous Accumulator

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
```

```
entity accumulator is
```

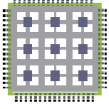

```
port(clk, reset : in std_logic;
Din : in std_logic_vector(3 downto 0);
Q : out std_logic_vector(3 downto 0));
end accumulator;
architecture bhv of accumulator is
signal tmp: std_logic_vector(3 downto 0);
begin
process (clk, reset)
begin
if (reset='1') then
tmp <= "0000";
elsif rising_edge(clk) then
tmp <= tmp + Din;
end if;
end process;
Q <= tmp;
end bhv;
```


TestBench VHDL Code for 4-bit Asynchronous Accumulator

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY tb_accumulator IS
END tb_accumulator;

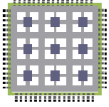ARCHITECTURE behavior OF tb_accumulator IS
```



```
-- Component Declaration for the Unit Under Test (UUT)

COMPONENT accumulator
PORT(
clk : IN std_logic;
reset : IN std_logic;
Din : IN std_logic_vector(3 downto 0);
Q : OUT std_logic_vector(3 downto 0)
);
END COMPONENT;

--Inputs
signal clk : std_logic := '0';
signal reset : std_logic := '0';
signal Din : std_logic_vector(3 downto 0) := (others => '0');


--Outputs
signal Q : std_logic_vector(3 downto 0);

-- Clock period definitions
constant clk_period : time := 20 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: accumulator PORT MAP (
  clk => clk,
  reset => reset,
  Din => Din,
  Q => Q
 );

 -- Clock process definitions
clk_process :process
```



```
begin
  clk <= '0';
  wait for clk_period/2;
  clk <= '1';
  wait for clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
  -- hold reset state for 100 ns.
  wait for 100 ns;

  reset <= '1';

  Din <= "0010";

  wait for 100 ns;

  reset <= '0';

  wait;

end process;

END;
```

Output Waveform for Accumulator VHDL Code

