



Contents

- [1 DeMultiplexer](#)
- [2 1 to 4 Demux](#)
- [3 Truth table for Demux 1 to 4](#)
- [4 1 to 4 Demux design using Logic Gates](#)
- [5 VHDL Code for 1 to 4 Demux](#)
- [6 VHDL Testbench Code for 1 to 4 Demux](#)
- [7 Testbench waveform for 1 to 4 Demux](#)

DeMultiplexer

Demultiplexer (DEMUX) select one output from the multiple output line and fetch the single input through selection line. It consist of 1 input and 2^n output. The output data lines are controlled by n selection lines. For Example, if $n = 2$ then the demux will be of 1 to 4 mux with 1 input, 2 selection line and 4 output as shown below. Also VHDL Code for 1 to 4 Demux described below.



1 to 4 Demux

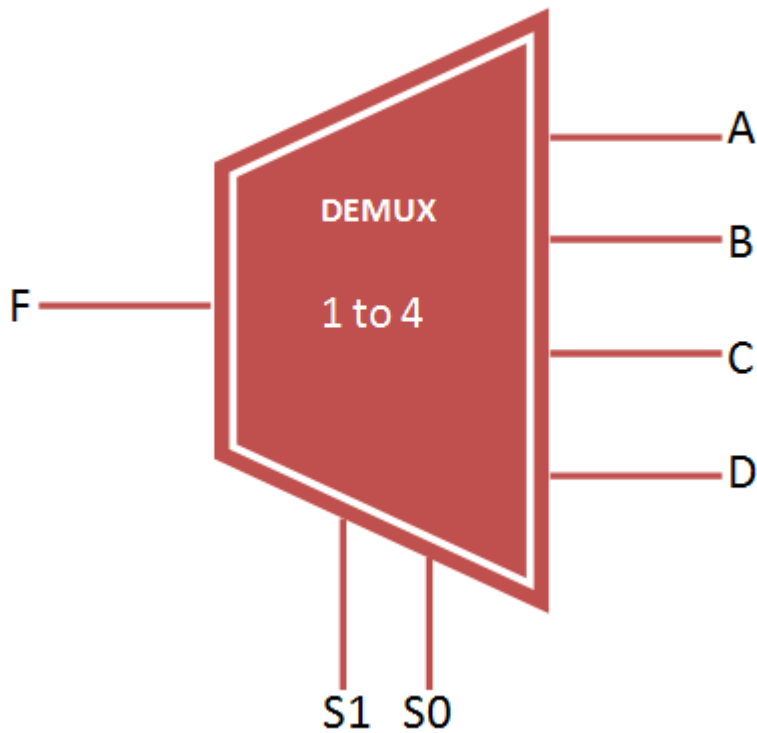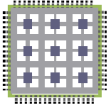

Truth table for Demux 1 to 4

Input	Selection line		Output			
F	S1	S0	D	C	B	A
1	0	0	0	0	0	1
1	0	0	0	0	1	0
1	0	0	0	1	0	0
1	0	0	1	0	0	0
0	X	X	0	0	0	0


1 to 4 Demux design using Logic Gates

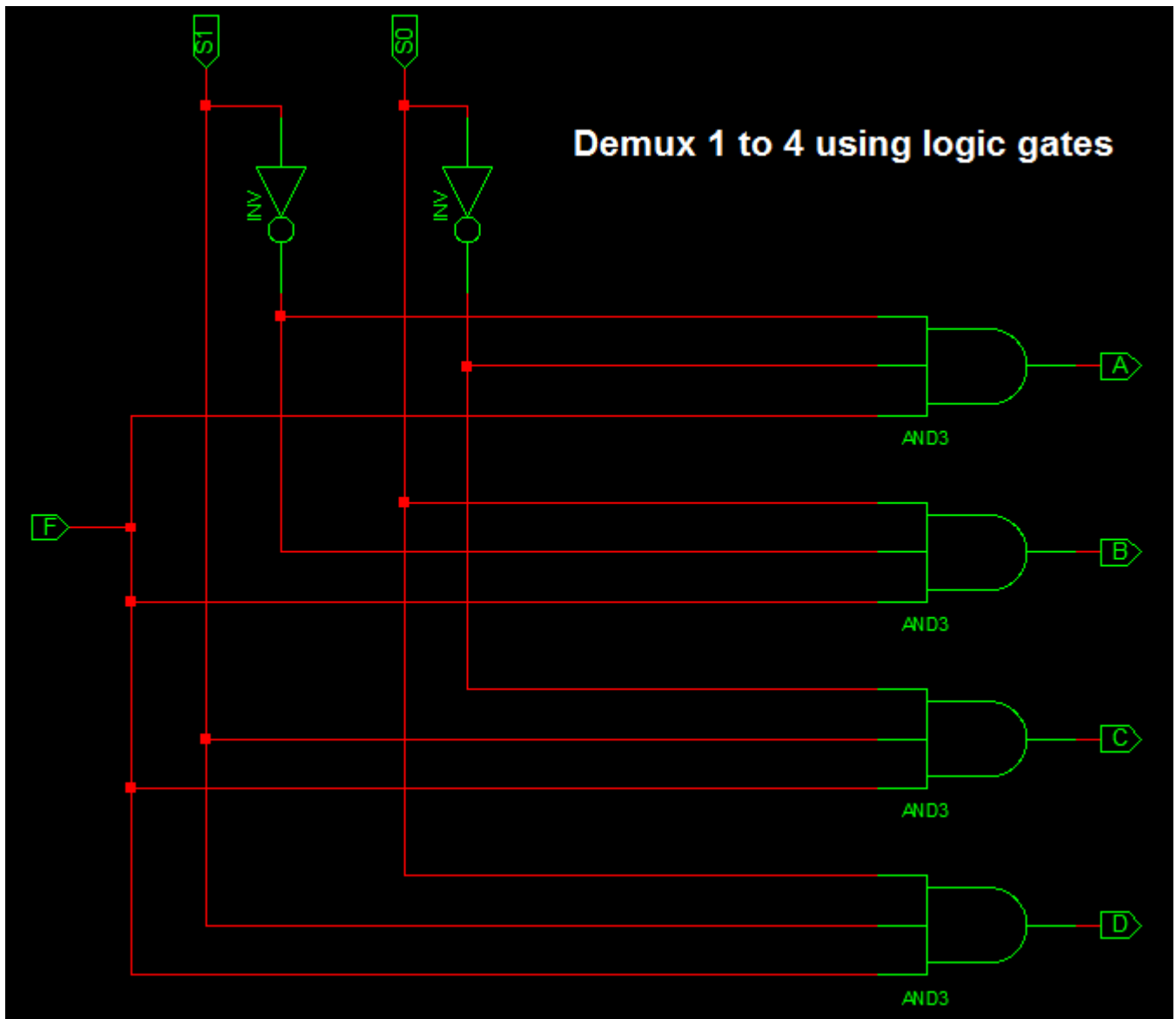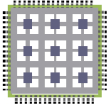

VHDL Code for 1 to 4 Demux

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity demux_1to4 is
port(
```

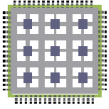

```
F : in STD_LOGIC;
S0,S1: in STD_LOGIC;
A,B,C,D: out STD_LOGIC
);
end demux_1to4;


architecture bhv of demux_1to4 is
begin
process (F,S0,S1) is
begin
if (S0 ='0' and S1 = '0') then
A <= F;
elsif (S0 ='1' and S1 = '0') then
B <= F;
elsif (S0 ='0' and S1 = '1') then
C <= F;
else
D <= F;
end if;

end process;
end bhv;
```

VHDL Testbench Code for 1 to 4 Demux

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_demux IS
END tb_demux;
```

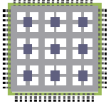

```
ARCHITECTURE behavior OF tb_demux IS

-- Component Declaration for the Unit Under Test (UUT)


COMPONENT demux_1to4
PORT(
F : IN std_logic;
S0 : IN std_logic;
S1 : IN std_logic;
A : OUT std_logic;
B : OUT std_logic;
C : OUT std_logic;
D : OUT std_logic
);
END COMPONENT;

--Inputs
signal F : std_logic := '0';
signal S0 : std_logic := '0';
signal S1 : std_logic := '0';


--Outputs
signal A : std_logic;
signal B : std_logic;
signal C : std_logic;
signal D : std_logic;
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

BEGIN

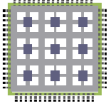-- Instantiate the Unit Under Test (UUT)
 uut: demux_1to4 PORT MAP (
F => F,
```




```
S0 => S0,  
S1 => S1,  
A => A,  
B => B,  
C => C,  
D => D  
);  
  
-- Stimulus process  
stim_proc: process  
begin  
-- hold reset state for 100 ns.  
wait for 100 ns;  
  
F <= '1';  
  
S0 <= '0'; S1 <= '0';  
  
wait for 100 ns;  
  
S0 <= '1'; S1 <= '0';  
  
wait for 100 ns;  
  
S0 <= '0'; S1 <= '1';  
  
wait for 100 ns;  
  
S0 <= '1'; S1 <= '1';  
  
wait for 100 ns;  
-- insert stimulus here  
  
wait;
```

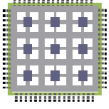

```
end process;
```

```
END;
```

Testbench waveform for 1 to 4 Demux

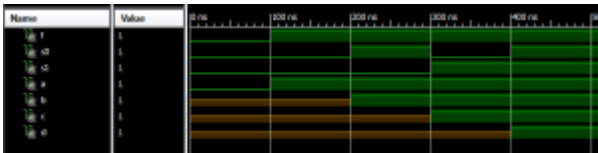

The above waveform represent the result of VHDL Code for 1 to 4 Demux.