

## Contents

- [1 Binary to BCD Converter](#)
- [2 VHDL Code for Binary to BCD Converter](#)
- [3 VHDL Teshbench Code for Binary to BCD Converter](#)
- [4 Simulation Waveform Result for Binary to BCD Converter](#)

## Binary to BCD Converter

Some times we need to display the output in a seven-segment display. For that purpose we will convert binary to BCD.


To translate from binary to BCD, we can employ the shift-and-add-3 algorithm:

Left-shift the (n-bit) binary number one bit.

If n shifts have taken place, the number has been fully expanded, so exit the algorithm.

If the binary value of any of the BCD columns is greater than or equal to 5, add 3.


Return to (1).

 

VHDL Code for Binary to BCD Converter
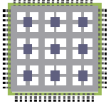
## VHDL Code for Binary to BCD Converter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
```




```
entity binary_bcd is
    generic(N: positive := 16);
    port(
        clk, reset: in std_logic;
        binary_in: in std_logic_vector(N-1 downto 0);
        bcd0, bcd1, bcd2, bcd3, bcd4: out std_logic_vector(3 downto 0)
    );
end binary_bcd ;

architecture behaviour of binary_bcd is
    type states is (start, shift, done);
    signal state, state_next: states;

    signal binary, binary_next: std_logic_vector(N-1 downto 0);
    signal bcds, bcds_reg, bcds_next: std_logic_vector(19 downto 0);
    -- output register keep output constant during conversion
    signal bcds_out_reg, bcds_out_reg_next: std_logic_vector(19 downto
0);
    -- need to keep track of shifts
    signal shift_counter, shift_counter_next: natural range 0 to N;
begin

    process(clk, reset)
    begin
        if reset = '1' then
            binary <= (others => '0');
            bcds <= (others => '0');
            state <= start;
            bcds_out_reg <= (others => '0');
            shift_counter <= 0;
        elsif falling_edge(clk) then
            binary <= binary_next;
            bcds <= bcds_next;
            state <= state_next;
        end if;
    end process;
end architecture;
```

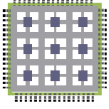


```
        bcds_out_reg <= bcds_out_reg_next;
        shift_counter <= shift_counter_next;
    end if;
end process;

convert:
process(state, binary, binary_in, bcds, bcds_reg, shift_counter)
begin
    state_next <= state;
    bcds_next <= bcds;
    binary_next <= binary;
    shift_counter_next <= shift_counter;

    case state is
        when start =>
            state_next <= shift;
            binary_next <= binary_in;
            bcds_next <= (others => '0');
            shift_counter_next <= 0;
        when shift =>
            if shift_counter = N then
                state_next <= done;
            else
                binary_next <= binary(N-2 downto 0) & 'L';
                bcds_next <= bcds_reg(18 downto 0) & binary(N-1);
                shift_counter_next <= shift_counter + 1;
            end if;
        when done =>
            state_next <= start;
    end case;
end process;

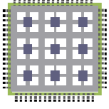    bcds_reg(19 downto 16) <= bcds(19 downto 16) + 3 when bcds(19
downto 16) > 4 else
```



```
                bcds(19 downto 16);
    bcds_reg(15 downto 12) <= bcds(15 downto 12) + 3 when bcds(15
downto 12) > 4 else
                bcds(15 downto 12);
    bcds_reg(11 downto 8) <= bcds(11 downto 8) + 3 when bcds(11 downto
8) > 4 else
                bcds(11 downto 8);
    bcds_reg(7 downto 4) <= bcds(7 downto 4) + 3 when bcds(7 downto 4)
> 4 else
                bcds(7 downto 4);
    bcds_reg(3 downto 0) <= bcds(3 downto 0) + 3 when bcds(3 downto 0)
> 4 else
                bcds(3 downto 0);

    bcds_out_reg_next <= bcds when state = done else
                bcds_out_reg;


    bcd4 <= bcds_out_reg(19 downto 16);
    bcd3 <= bcds_out_reg(15 downto 12);
    bcd2 <= bcds_out_reg(11 downto 8);
    bcd1 <= bcds_out_reg(7 downto 4);
    bcd0 <= bcds_out_reg(3 downto 0);

end behaviour;
```

## VHDL Teshbench Code for Binary to BCD Converter

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_bcd IS
END tb_bcd;
```

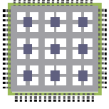

```
ARCHITECTURE behavior OF tb_bcd IS

    -- Component Declaration for the Unit Under Test (UUT)


    COMPONENT binary_bcd
    PORT(
        clk : IN  std_logic;
        reset : IN  std_logic;
        binary_in : IN  std_logic_vector(15 downto 0);
        bcd0 : OUT  std_logic_vector(3 downto 0);
        bcd1 : OUT  std_logic_vector(3 downto 0);
        bcd2 : OUT  std_logic_vector(3 downto 0);
        bcd3 : OUT  std_logic_vector(3 downto 0);
        bcd4 : OUT  std_logic_vector(3 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal clk : std_logic := '0';
    signal reset : std_logic := '0';
    signal binary_in : std_logic_vector(15 downto 0) := (others =>
'0');

        --Outputs
    signal bcd0 : std_logic_vector(3 downto 0);
    signal bcd1 : std_logic_vector(3 downto 0);
    signal bcd2 : std_logic_vector(3 downto 0);
    signal bcd3 : std_logic_vector(3 downto 0);
    signal bcd4 : std_logic_vector(3 downto 0);

    -- Clock period definitions
    constant clk_period : time := 10 ns;

BEGIN
```

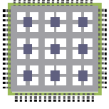


```
-- Instantiate the Unit Under Test (UUT)
 uut: binary_bcd PORT MAP (
     clk => clk,
     reset => reset,
     binary_in => binary_in,
     bcd0 => bcd0,
     bcd1 => bcd1,
     bcd2 => bcd2,
     bcd3 => bcd3,
     bcd4 => bcd4
 );

-- Clock process definitions
 clk_process :process
 begin
     clk <= '0';
     wait for clk_period/2;
     clk <= '1';
     wait for clk_period/2;
 end process;

-- Stimulus process
 stim_proc: process
 begin
     -- hold reset state for 100 ns.
     reset <= '1';
     wait for 100 ns;
     reset <= '0';

     binary_in <= "0000000000001111";
     wait for 200 ns;

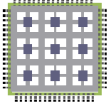     binary_in <= "0000000001001111";
     wait for 200 ns;
```



```
        binary_in <= "0000000001111111";  
    wait for 200 ns;  
  
        binary_in <= "0000111101001111";  
    wait for 2000 ns;  
  
end process;  
  
END;
```

## Simulation Waveform Result for Binary to BCD Converter

